

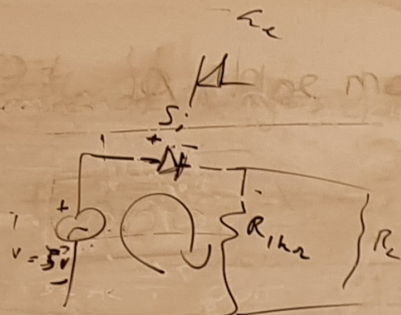
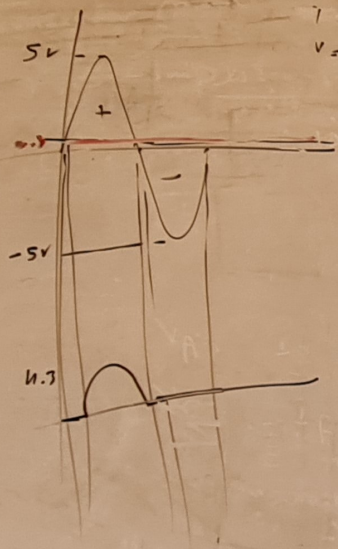


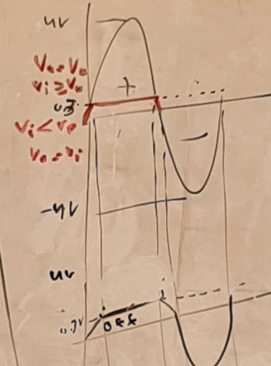

At (+) 1/2 cycle
 Diode (F)
 on (sh.c)
 ($I = \max, V = 0$)

by (k.v.l)
 $\sum V_i = \sum V_o = V_i - V_D = V_o$
 $= 5 - 0.7 \Rightarrow V_o = \boxed{4.3V}$


CLIPPER

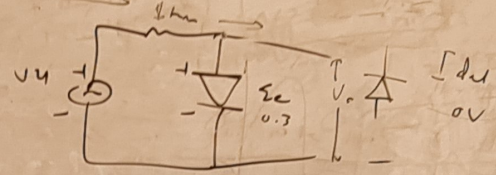

At (+) 1/2 cycle
 D (R)
 off (O.P.C)
 $I = 0$
 $V = IR$
 $V_o = 0$


At (+) 1/2 cycle
 D is (F)
 D on
 If $V_i < V_D$
 $V_o = V_i$
 If $V_i \geq V_D$
 $V_o = V_D$

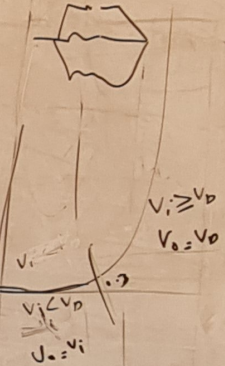At (-) 1/2 cycle
 D is R
 D off
 $V_o = V_i$
 $V_o = -4V$



CYA

Q1.

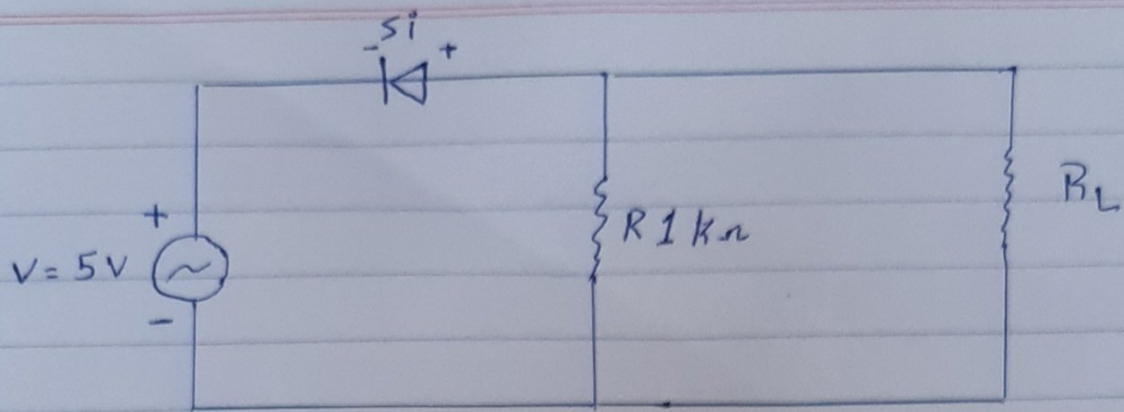

Q2.

