

# Questions


- Design Combinational Circuit

With 3-inputs and 1-output (F)

the output (F) equal 0; if the  
sum of input  $\geq 2$ ,

Get the Logic Function?

| a | b | c | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |

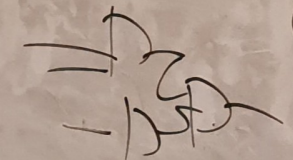

24x10<sup>6</sup> m/s